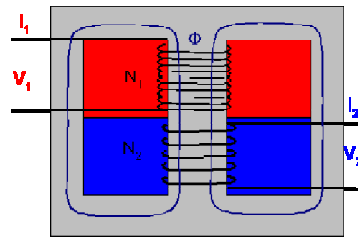


7. Transformers

- 7.1 What does one look like?
- 7.2 How does it work?
- 7.3 What is the model?
- 7.4 How does one find the parameters?
- 7.5 How are transformers used?
- 7.6 What's missing?

7.1 What does one look like?

- Primary winding
 - V_1, I_1, N_1
- Secondary winding
 - V_2, I_2, N_2
 - HV & LV
- Core
 - Flux Φ links 1 and 2



7.2 How does it work?


- Simplified Approach- *IDEAL* Transformer:
- Flux, EMF:
 - AC Voltage, V_1 applied to primary, secondary OC.
 - Small AC current, I_0 , flows $\Rightarrow \mathcal{F}_0 \Rightarrow \Phi$.
 - $E_1 = N_1 d\Phi/dt = 4.44 f N_1 \Phi \approx V_1$.
 - $E_2 = N_2 d\Phi/dt = 4.44 f N_2 \Phi \approx V_2$.
 - $V_1/V_2 = N_1/N_2 = k$

Transformer action

- Balance of Ampere Turns:
- Load R_2 .
- I_2 flows $\Rightarrow \mathcal{F}_2 \Rightarrow$ decrease in $\Phi \Rightarrow \downarrow E_1$.
- BUT $E_1 \approx V_1$ so $\uparrow I_1$, such that $\mathcal{F}_1 = \mathcal{F}_2$.
- $N_1 I_1 = N_2 I_2$
- $I_1 / I_2 = N_2 / N_1 = 1/k$
- Effective load on primary: R'_2 :
- $R'_2 = V_1 / I_2 = k V_2 / (I_2 / k) = k^2 V_2 / I_2$.
- $R'_2 = k^2 R_2$

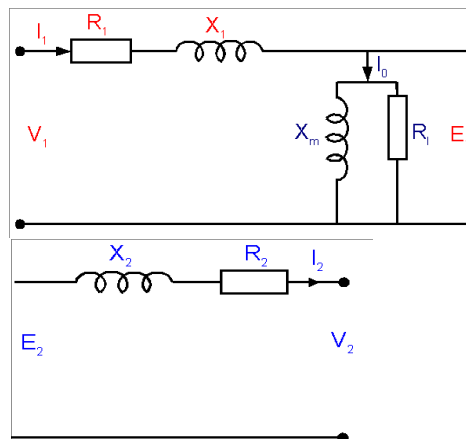7.3 What is the model?

- Primary
 - R_1
 - X_1
 - X_m or B
 - R_l or G
- Secondary
 - X_2
 - R_2




Full equivalent circuit

- Refer primary to secondary (can also refer to primary)


$E_1 = E'_2$.
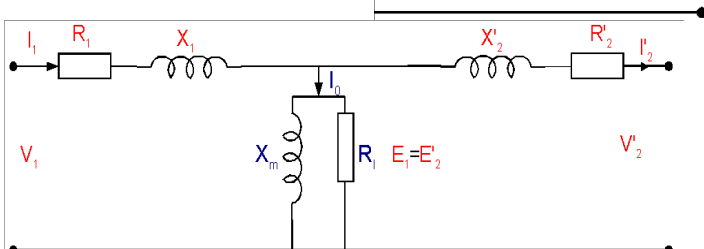
$$\begin{aligned} X'_2 &= k^2 X_2 & R'_2 &= k^2 R_2 \\ E'_2 &= k E_2 & V'_2 &= k V_2 \\ I'_2 &= I_2 / k \end{aligned}$$



Approximate Equivalent Circuit

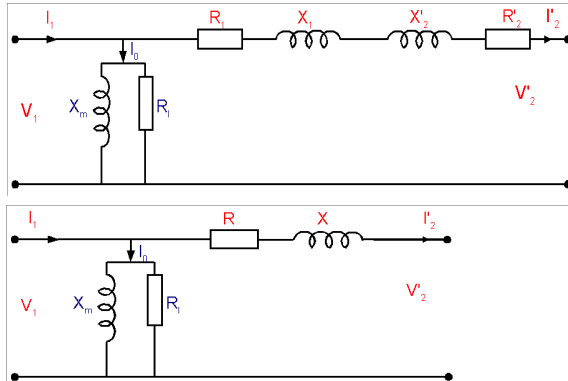If $R_1, X_1 \ll X_m, R_1$ then move parallel branch to left.




7.4 How does one find the parameters?

Open circuit test (LV)

$$R_1 = \frac{V^2}{P}$$

$$I_x = \sqrt{I^2 - \left(\frac{V}{R_1}\right)^2}$$

$$X = \frac{V}{I_x}$$

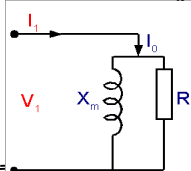


Short Circuit test (HV)

$$R = \frac{P}{I^2}$$

$$Z = \frac{V}{I}$$

$$X = \sqrt{Z^2 - R^2}$$

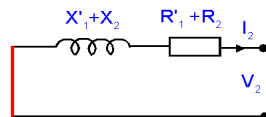

7.5 How are transformers used?

- Ratings
- Performance parameters
- Three Phase connections
- Special Transformers



Ratings

Rating is NOT necessarily operating condition.

Main (Nameplate)

Voltage

VA

Secondary

Frequency

% Impedance = $\frac{I_{Rated}}{I_{SC}} * 100$

$Z = V_p / I_{SC}$

Performance parameters

Efficiency

$$\eta = \frac{P_{Out}}{P_{In}} = \frac{P_{Out}}{(P_{Out} + P_{Cu} + P_{Fe})}$$

$$\eta = \frac{P_{out}}{(P_{out} + I^2 R + P_{Fe})}$$

$$\eta_{max} \Rightarrow P_{Cu} = P_{Fe}, \text{unity pf}$$

% Regulation:

$$\frac{V_{NL} - V_L}{V_{NL}} * 100$$

Three Phase connections

3 single phase transformers or 1 three phase

Connections:

Star-star

Delta - delta

Star-delta, delta-star

Always work in PHASE quantities. Remember $\sqrt{3}$

Special Transformers

- ✎ Power transformer
- ✎ Distribution
- ✎ Welding

Example

- ✎ A 500 kVA, 3 Phase 22kV, 11kV star-star transformer has a no load current of 1.1A. It has a maximum efficiency of 96% when operating at rated load, unity power factor. The short circuit current is 8 times rated current.
- ✎ Determine:
 - ✎ the parameters of the approximate equivalent circuit.
 - ✎ the regulation when supplying 80% rated current at 0.8 pf lag

Solution

- ✎ $V_p^* = 22k/\sqrt{3} = 12.7 \text{ kV}$ $I_p^* = S/3V_p = 500/12.7 = 39.4 \text{ A}$
- ✎ Approximate Circuit
 - ✎ $P_{\text{Out}} + 2P_{\text{fe}} = P_{\text{Out}}/\eta \Rightarrow P_{\text{fe}} = 0.5(1/\eta - 1)P_{\text{Out}} = 10 \text{ kW}$
 - ✎ $R_1 = 3V_p^2 / P_{\text{fe}} = 3 \cdot 12710^2 / (10000) = 48.5 \text{ k}\Omega$
 - ✎ $I_R = V_p / R_1 = 0.26 \text{ A}$
 - ✎ $X_M = V_p / \sqrt{(I_0^2 - I_R^2)} = 12700 / \sqrt{(1.1^2 - 0.26^2)} = 11.9 \text{ k}\Omega$
 - ✎ $R = P_{\text{cu}} / 3I_p^2 = 10000 / (3 \cdot 39.4^2) = 2.1 \Omega$
 - ✎ $Z = V_p / (8 I_p) = 12700 / (8 \cdot 39.4) = 40.3 \Omega$
 - ✎ $X = \sqrt{(Z^2 - R^2)} = 40.2 \Omega$

Solution part 2

- ✎ Solve for V'_2 : $V_1 = 12.7 \text{ kV}$ $I = 0.8 \cdot 39.4 = 31.5 \text{ A}$
- ✎ $V_1 \angle \alpha = V'_2 \angle 0 + I \angle -36.8 (R + jX)$
- ✎ Imaginary: $V_1 \sin \alpha = IR \sin -36.8 + IX \cos -36.8$
- ✎ $\alpha = \sin^{-1}((-39.6 + 1014)/12700) = 4.8^\circ$
- ✎ Real: $V_2 \cos \alpha = V'_2 + IR \cos -36.8 - IX \sin -36.8$
- ✎ $V'_2 = V_2 \cos \alpha - IR \cos -36.8 + IX \sin -36.8 = 11.9 \text{ kV}$
- ✎ Regulation: $(12.7 - 11.9)/12.7 = 6.3\%$

7.6 What's missing?

- ✎ Alternative connections
- ✎ Saturation
- ✎ Inrush currents
- ✎ Interwinding capacitance
- ✎ Zig-zag windings etc.